

# Chapter 4 Designing Combinational Systems

---

- Full adder
- Ripple carry adders
- Carry look-ahead adders
- Decoder
- Multiplexer
- Buffer
- Bus
- Gate arrays
  - ROM
  - PLA
  - PAL

# Full Adder

$x_i$	$y_i$	$C_i$	$C_{i+1}$	$S_i$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

(a) Truth table for full adder

$c_i \backslash x_i y_i$	00	01	11	10
0		<b>1</b>		<b>1</b>
1	<b>1</b>		<b>1</b>	


$$S_i = x_i \oplus y_i \oplus c_i$$

$c_i \backslash x_i y_i$	00	01	11	10
0			<b>1</b>	
1		<b>1</b>	<b>1</b>	<b>1</b>


$$c_{i+1} = x_i y_i + c_i (x_i \oplus y_i)$$

(b) Map representation

# Full Adder

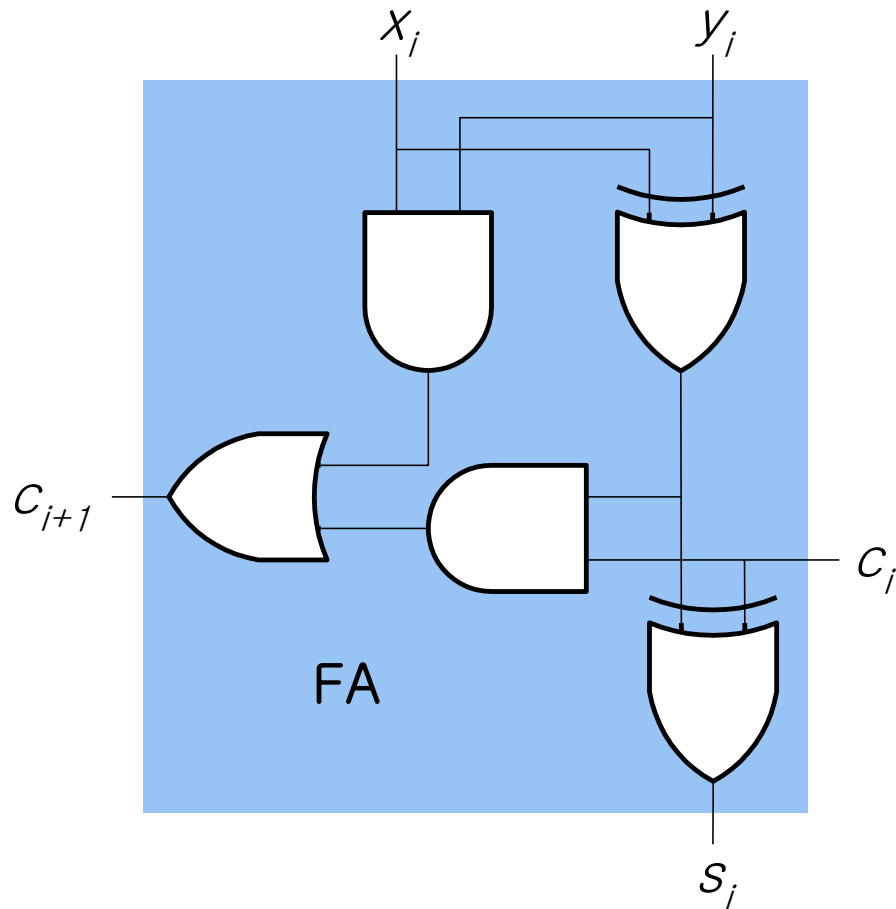


(c) Full-adder logic schematic

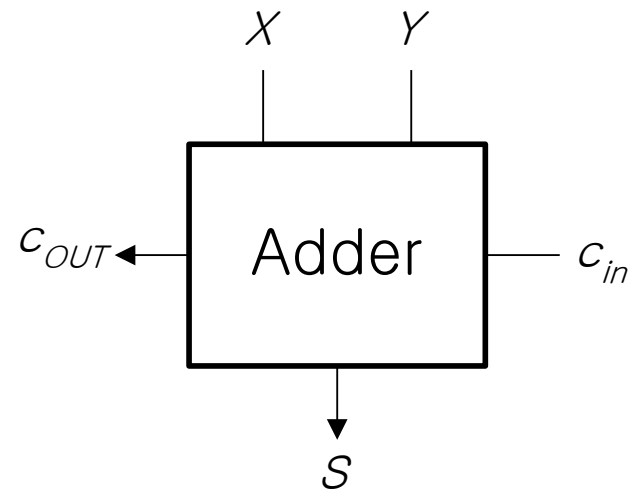


(e) Graphic symbol

# Gate delay

**Figure 4.2** Illustration of gate delay.

 


(a)

 

(b)

# Delay through 1-bit adder (full adder)


**Figure 4.3** Delay through a 1-bit adder.

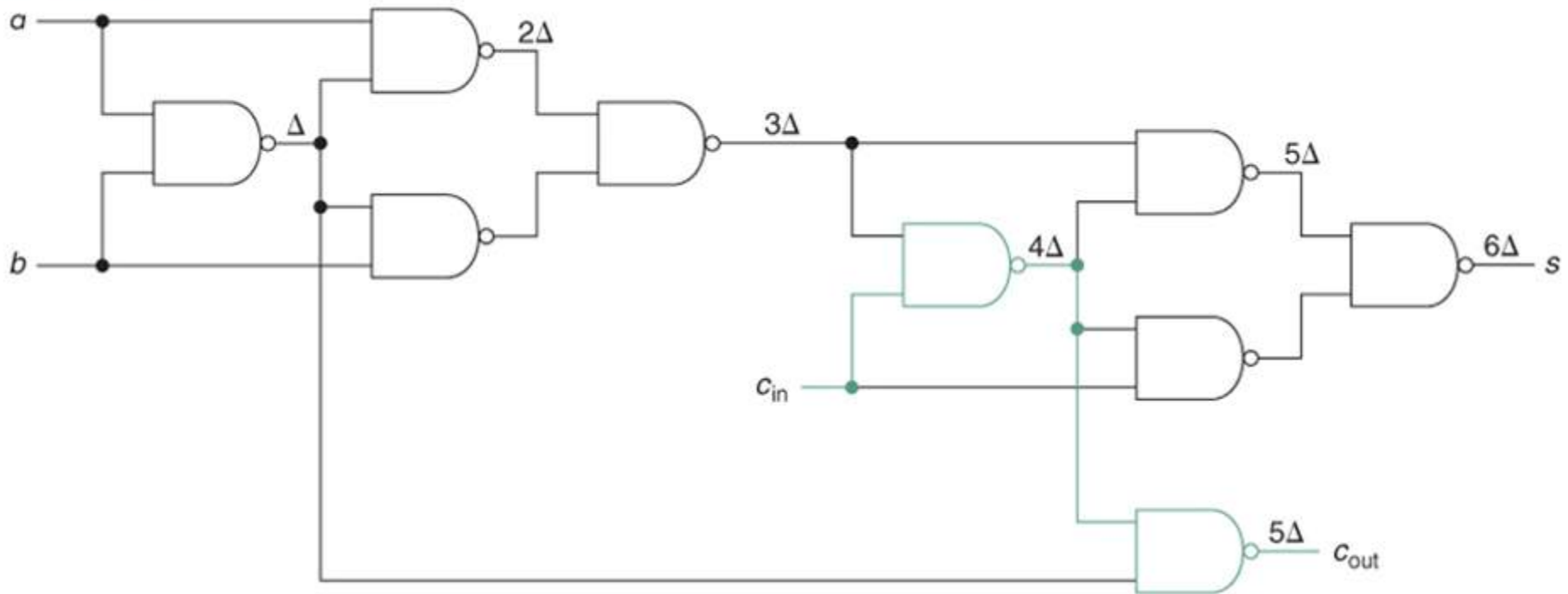


N-bit adder can be built by connecting  $n$  1-bit adders (ripple carry adder)  
Time for  $n$ -bit adder =  $(2n+4)\Delta$

# 4-bit ripple carry adder

**Figure 4.1** A 4-bit adder.

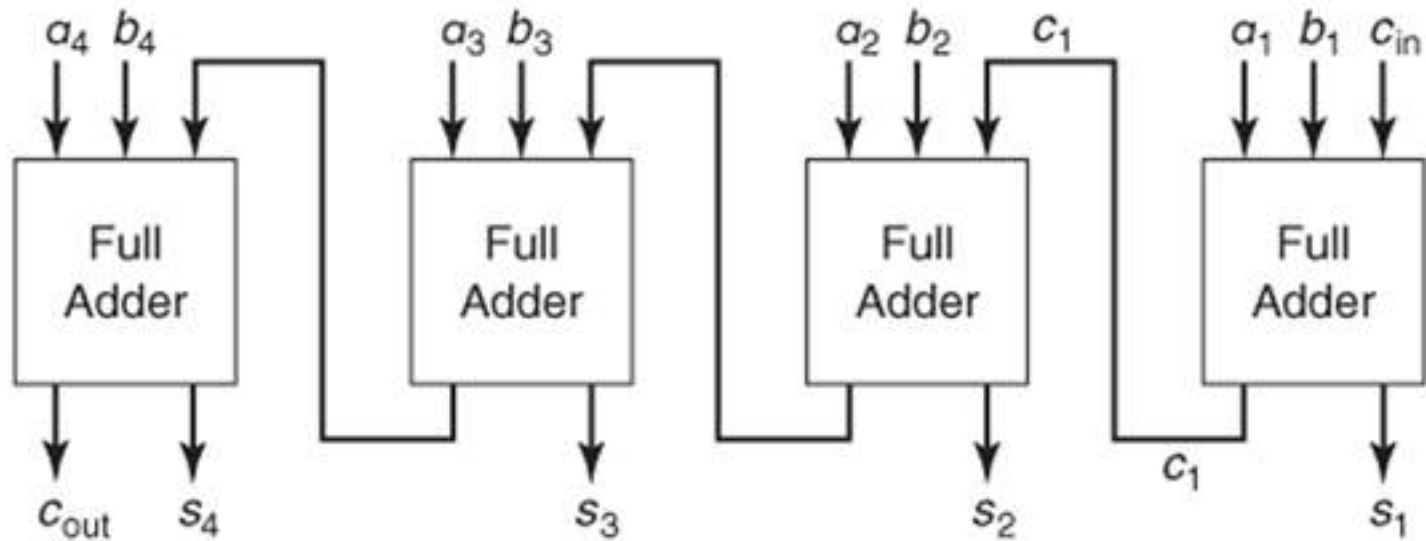

# 8-bit Ripple carry adder

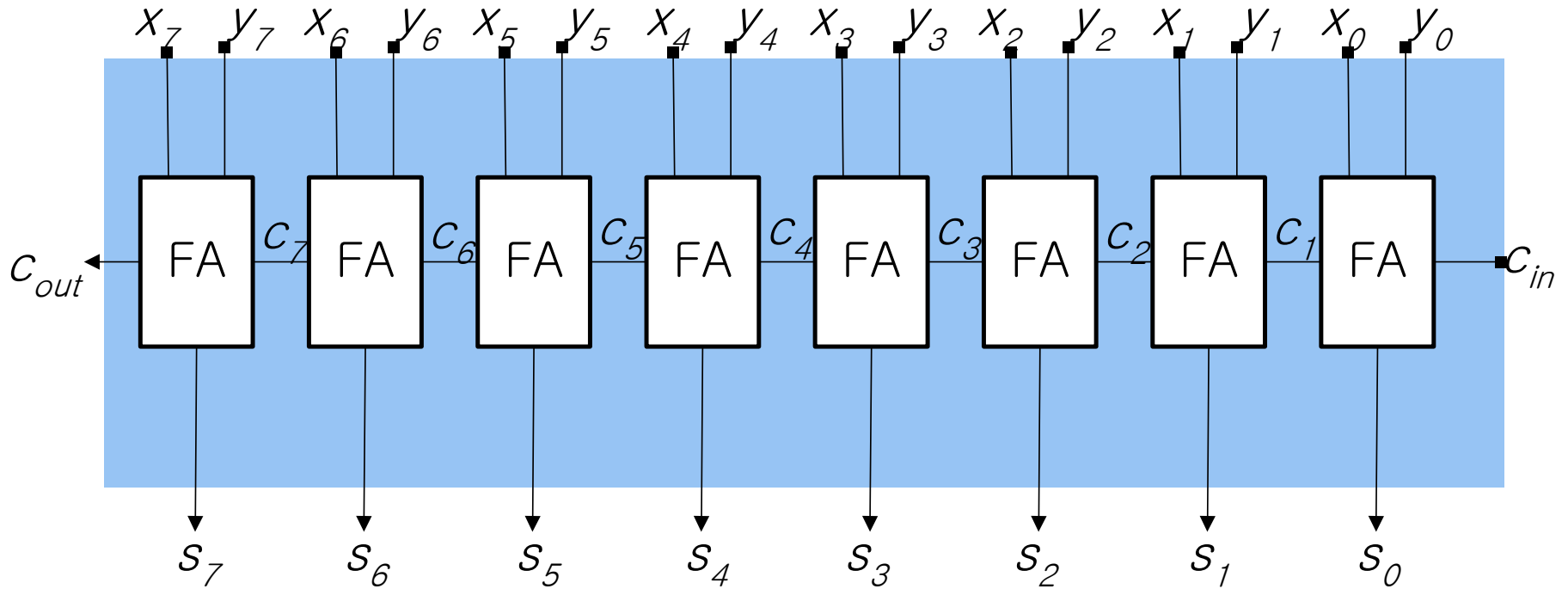

# Carry look-ahead adders

---

## ■ Advantage of Carry-look-ahead technique

- **reduce the delay of the carry chain** in this kind of ripple-carry chain

## ■ $x_{i+3}x_{i+2}x_{i+1}x_i + y_{i+3}y_{i+2}y_{i+1}y_i$ (input carry $c_i$ )

- carry-generate function  $g_i = x_i y_i$
- carry-propagate function  $p_i = x_i \oplus y_i$
- $c_{i+1} = g_i + p_i c_i$                        $c_{i+2} = g_{i+1} + p_{i+1} c_{i+1}$   
 $c_{i+3} = g_{i+2} + p_{i+2} c_{i+2}$                $c_{i+4} = g_{i+3} + p_{i+3} c_{i+3}$

## ■ Express in terms of $c_i$

- $c_{i+1} = g_i + p_i c_i$   
 $c_{i+2} = g_{i+1} + p_{i+1} g_i + p_{i+1} p_i c_i$   
 $c_{i+3} = g_{i+2} + p_{i+2} g_{i+1} + p_{i+2} p_{i+1} g_i + p_{i+2} p_{i+1} p_i c_i$   
 $c_{i+4} = g_{i+3} + p_{i+3} g_{i+2} + p_{i+3} p_{i+2} g_{i+1} + p_{i+3} p_{i+2} p_{i+1} g_i + p_{i+3} p_{i+2} p_{i+1} p_i c_i$   
 $\Rightarrow$  can compute directly from input bits and input carry  $c_i$



# Carry look-ahead adders

---


## ▪ carry-look-ahead(CLA) generator

- $c_{i+4} = g_{(i,i+3)} + p_{(i,i+3)}c_i$ 
  - $g_{(i,i+3)} = g_{i+3} + p_{i+3}g_{i+2} + p_{i+3}p_{i+2}g_{i+1} + p_{i+3}p_{i+2}p_{i+1}g_i$
  - $p_{(i,i+3)} = p_{i+3}p_{i+2}p_{i+1}p_i$
- **replace the 4-bit carry chain**, so make **the adder faster**

## ▪ carry-look-ahead adder v.s. ripple-carry-adder

- ripple-carry adder
  - consist of 4 FA carry chains
  - each FA carry chain consists of 1 AND and 1 OR gate, used to compute  $c_{i+1} = g_i + p_i c_i$
- carry-look-ahead adder
  - CLA generator can produce 4 carries with less delay than the ripple-carry chain
  - produce a faster 4-bit adder, and improve the speed of larger adders as well
 
# Carry generation of 4-bit ripple carry adder



- carry-generate function  $g_i = x_i y_i$
- carry-propagate function  $p_i = x_i \oplus y_i$


$$C_{i+1} = g_i + p_i C_i$$

$$C_{i+2} = g_{i+1} + p_{i+1} g_i + p_{i+1} p_i C_i$$


$$C_{i+3} = g_{i+2} + p_{i+2} g_{i+1} + p_{i+2} p_{i+1} g_i + p_{i+2} p_{i+1} p_i C_i$$

$$C_{i+4} = g_{i+3} + p_{i+3} g_{i+2} + p_{i+3} p_{i+2} g_{i+1} + p_{i+3} p_{i+2} p_{i+1} g_i + p_{i+3} p_{i+2} p_{i+1} p_i C_i$$

# 4-bit carry look-ahead adder

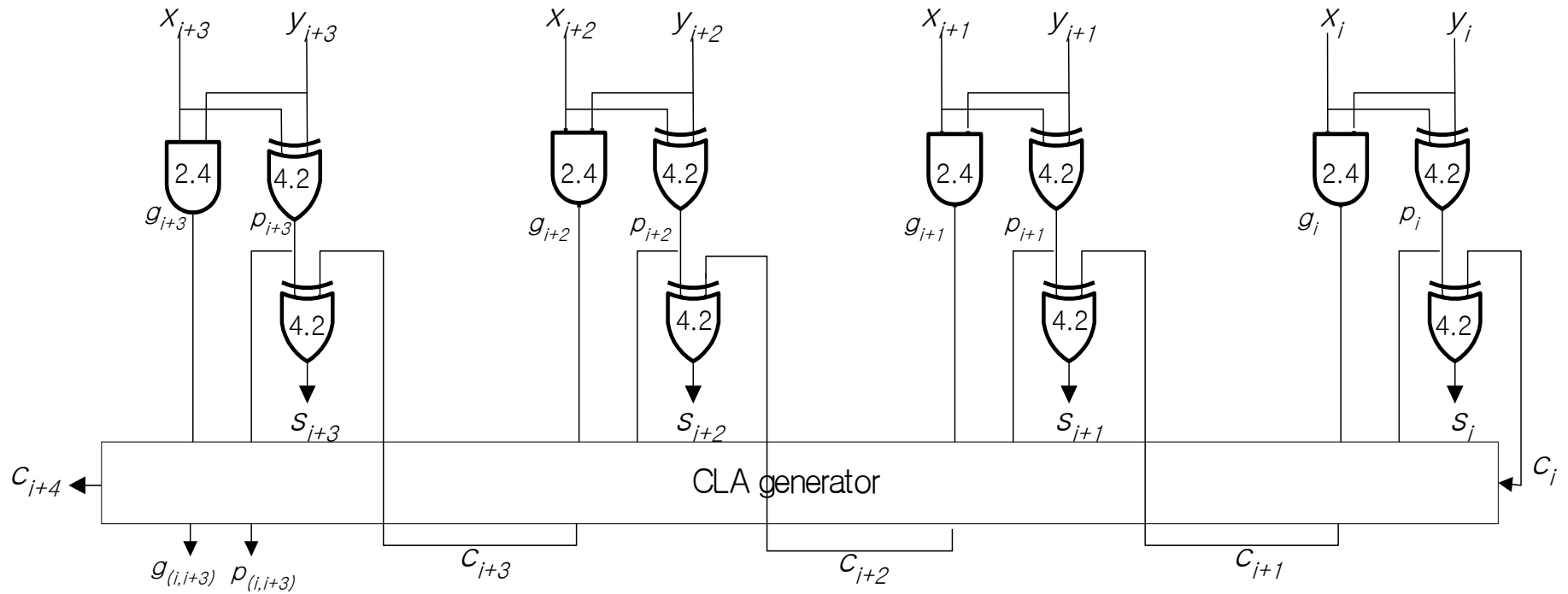

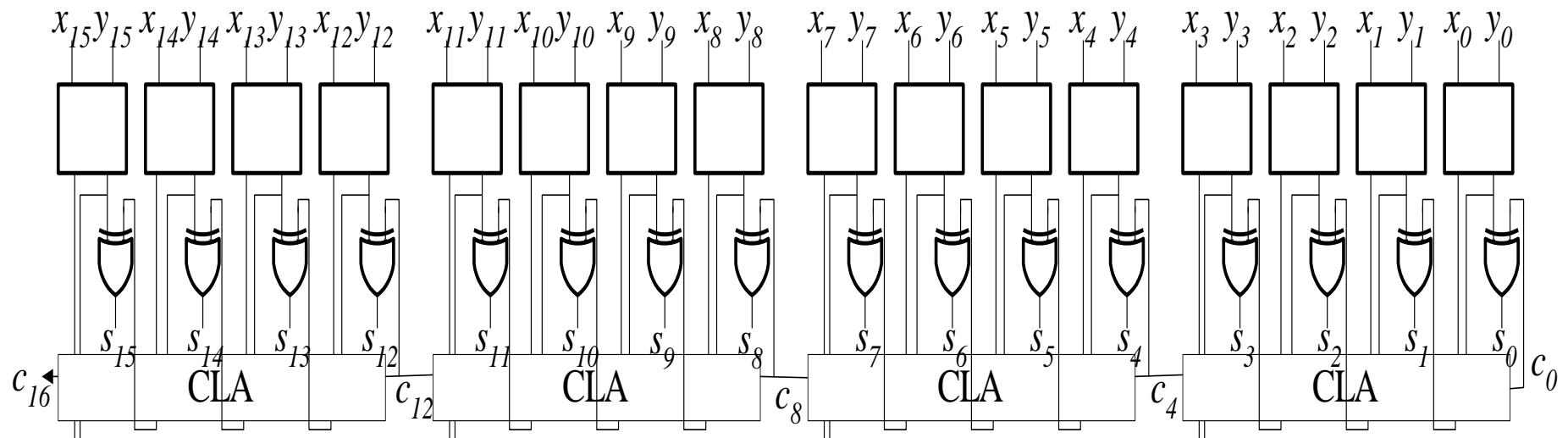
# Single-level 16-bit carry look-ahead adder



# 2-level 16-bit carry look-ahead adder
 
## ■ Two-level CLA generator

- speed up by using an additional CLA generator
- $c_4 = g_{(0,3)} + p_{(0,3)}c_0$        $c_8 = g_{(4,7)} + p_{(4,7)}c_4$   
 $c_{12} = g_{(8,11)} + p_{(8,11)}c_8$        $c_{16} = g_{(12,15)} + p_{(12,15)}c_{12}$
- second level generates these carries for the first-level CLA generator



(b) Two-level CLA generator

# Delay comparison

CARRY CHAIN	RIPPLE DELAY	ONE-LEVEL CLA	TWO-LEVEL CLA
$c_0(x_0, y_0)$ to $c_4$	19.2 (23.4)	4.8 (13.0)	4.8 (13.2)
$c_0(x_0, y_0)$ to $c_8$	38.4 (42.6)	9.6 (17.8)	5.6 (16.2)
$c_0(x_0, y_0)$ to $c_{12}$	57.6 (61.8)	14.4 (22.6)	6.4 (17.0)
$c_0(x_0, y_0)$ to $c_{16}$	76.8 (81.0)	19.2 (27.4)	4.8 (19.4)

delay from  
 $x_0$  or  $y_0$

# Adders/Subtractors

## ■ Binary subtraction


- add the minuend to the 2's complement of the subtrahend

## ■ Adders/Subtractor

- inputs :  $A = a_{n-1} \dots a_0$  and  $B = b_{n-1} \dots b_0$
- output :  $F = f_{n-1} \dots f_0$
- select signal :  $S$

S	FUNCTION	COMMENT
0	$A + B$	Addition
1	$A + B' + 1$	Subtraction

(a) Truth table

 

(b) Graphic symbol

Two's-complement adder/subtractor

# Adders/Subtractors

- Subtraction : Develop the truth table for a 1-bit full subtractor and cascade as many of these as are needed, producing a borrow-ripple subtractor.
- Adder/Subtractor : signal line = 0 for addition & signal line = 1 for subtraction.

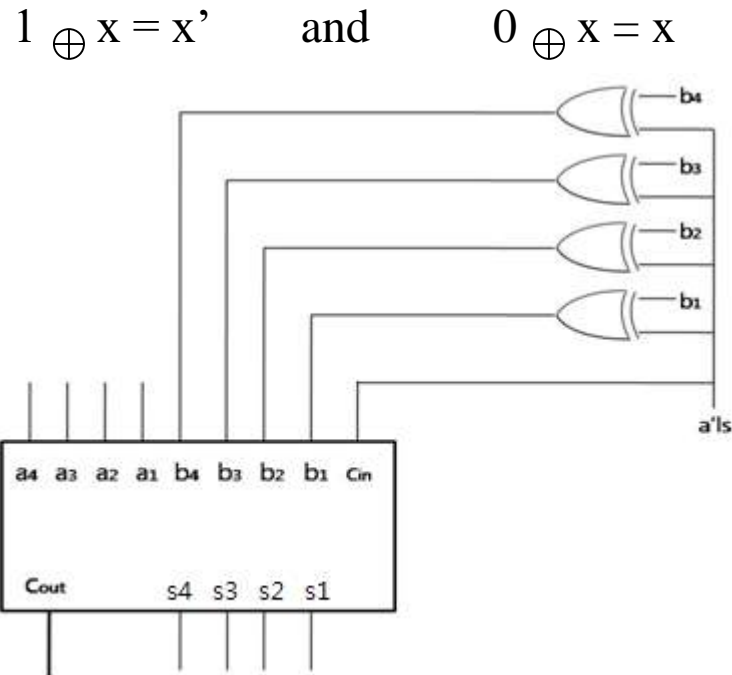


Figure 4.5




# Binary decoders

**Table 4.2a** An active high decoder.

<i>a</i>	<i>b</i>	<i>0</i>	<i>1</i>	<i>2</i>	<i>3</i>
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

**Figure 4.8a** An active high decoder.

 


# Binary decoders

**Table 4.2b** An active low decoder.



<i>a</i>	<i>b</i>	<i>0</i>	<i>1</i>	<i>2</i>	<i>3</i>
0	0	0	1	1	1
0	1	1	0	1	1
1	0	1	1	0	1
1	1	1	1	1	0

   **Figure 4.8b** An active low decoder.

 


**Figure 4.9** Decoder with enable.

$EN'$	$a$	$b$	0	1	2	3
1	X	X	0	0	0	0
0	0	0	1	0	0	0
0	0	1	0	1	0	0
0	1	0	0	0	1	0
0	1	1	0	0	0	1




# 3x8 decoder




a	b	c	$y_0$	$y_1$	$y_2$	$y_3$	$y_4$	$y_5$	$y_6$	$y_7$
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

# 4x16 decoder using 2x4 decoders

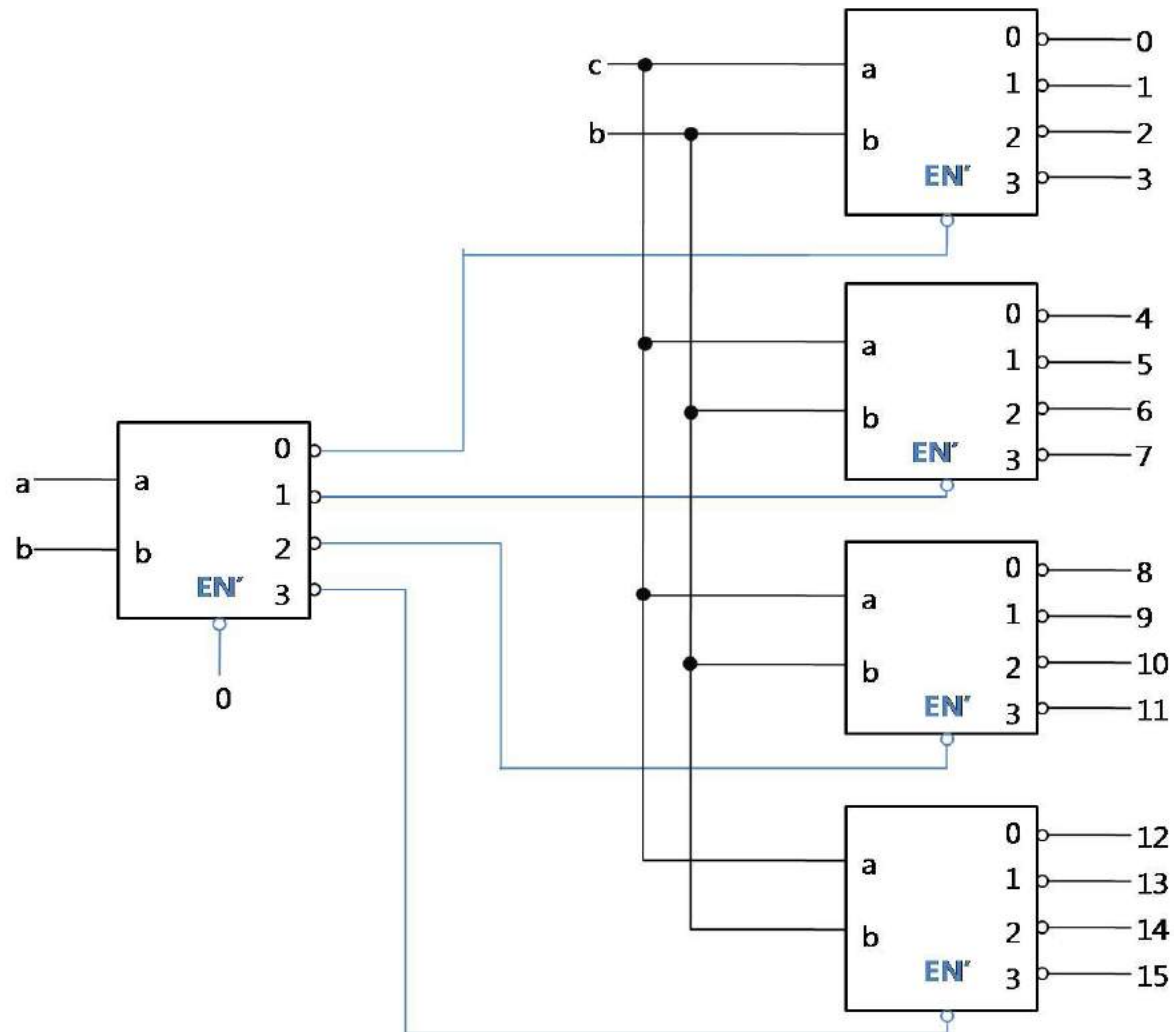


# Logic function by decoders

 - Example 4.3
  - Implementation of logic function
$$f(a, b, c) = \sum m(0, 2, 3, 7)$$
$$g(a, b, c) = \sum m(1, 4, 6, 7)$$


 
# Multiplexers (data selectors)

- combinatorial component that can select one of several data sources to be used as operands for an ALU
- $n$  inputs, one output,  $\log_2 n$  select signals




(a) Graphic symbol

$S$	$Y$
0	$D_0$
1	$D_1$

(b) Truth table


$$Y = S D_0 + S D_1$$

(c) Boolean expression

 

(d) Logic diagram

# 4x1 Multiplexer

 


(a) Graphic symbol

$S_1$	$S_0$	$Y$
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

(b) Truth table

$$Y = S_1 \bar{S}_0 D_0 + S_1 \bar{S}_0 D_1 + S_1 S_0 D_2 + S_1 S_0 D_3$$




(c) Boolean expression

 

(d) Logic diagram




# 4x1 MUX using 3 (2x1) MUX

   

# 8x1 Multiplexer (1)

$S_2$	$S_1$	$S_0$	$Y$
0	0	0	$D_0$
0	0	1	$D_1$
0	1	0	$D_2$
0	1	1	$D_3$
1	0	0	$D_4$
1	0	1	$D_5$
1	1	0	$D_6$
1	1	1	$D_7$

(a) Truth table

 


(b) Implementation with 2-to-1 selectors

## 8x1 multiplexer (2)


$S_2$	$S_1$	$S_0$	$Y$
0	0	0	$D_0$
0	0	1	$D_1$
0	1	0	$D_2$
0	1	1	$D_3$
1	0	0	$D_4$
1	0	1	$D_5$
1	1	0	$D_6$
1	1	1	$D_7$

(a) Truth table

 

(b) Implementation with a decoder

# Multi-bit multiplexer

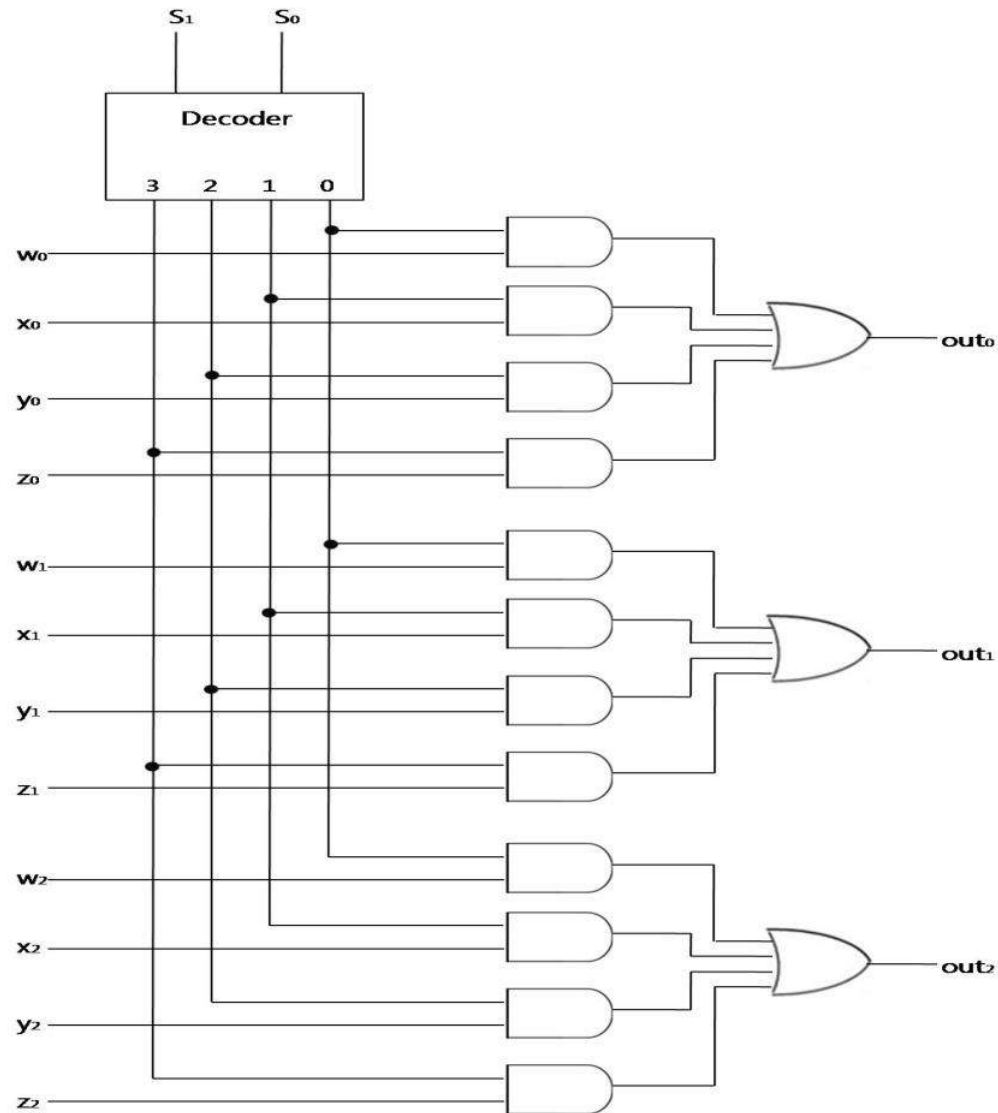


# Function implementation using mux

---

- Multiplexers can be used to implement logic functions.
- Example 4.4
  - Implement the function
$$f(a, b) = \sum m(0, 1, 3)$$

<i>a</i>	<i>b</i>	<i>f</i>
0	0	1
0	1	1
1	0	0
1	1	1

 

# Three state gates (buffers)

EN	a	F
0	0	Z
0	1	Z
1	0	0
1	1	1


 
 


Figure 4.15

- Three-state buffers with active low enables and/or outputs exist.
- Three-state outputs also exist on other more complex gates.
- A multiplexer using three-state gates. (without the OR gate)
  - The enable is the control input :  $f = a$  ( $EN = 0$ ) or  $f = b$  ( $EN = 1$ )
  - The three-state gate is often used for signals that travel between systems.
  - bus : it is a set of lines over which data is transferred.


# BUS

 

(a) Tristate driver symbol

$E$	$Y$
0	$Z$
1	$D$

(b) Truth table for tristate driver

 


(c) 2-input bus

$S$	$Y$
0	$D_0$
1	$D_1$

(d) Truth table for 2-input bus

# bus

 

(e) 4-input bus


$S_1$	$S_0$	$Y$
0	0	$D_0$
0	1	$D_1$
1	0	$D_2$
1	1	$D_3$

(f) Truth table for 4-input bus



# Read-Only Memory (ROM)

- An 8-Word x 4-Bit ROM

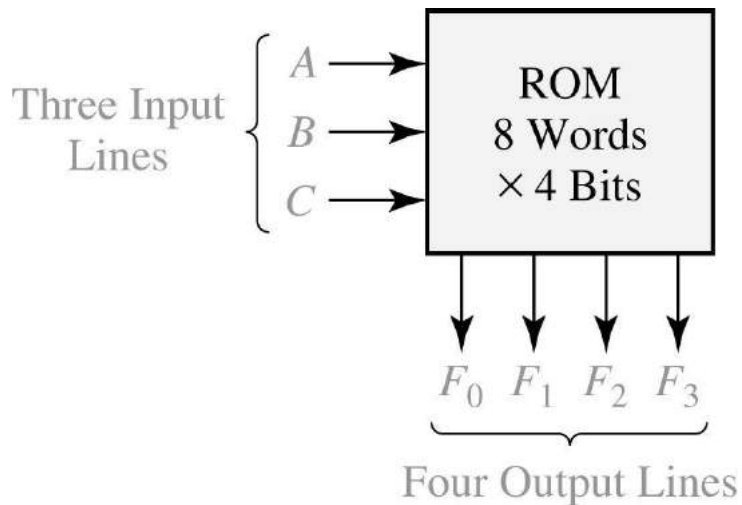

(a) Block diagram


A	B	C	$F_0$	$F_1$	$F_2$	$F_3$
0	0	0	1	0	1	0
0	0	1	1	0	1	0
0	1	0	0	1	1	1
0	1	1	0	1	0	1
1	0	0	1	1	0	0
1	0	1	0	0	0	1
1	1	0	1	1	1	1
1	1	1	0	1	0	1

typical data  
stored in  
ROM  
( $2^3$  words of  
4bits each)


(b) Truth table for ROM

# Basic ROM structure

---

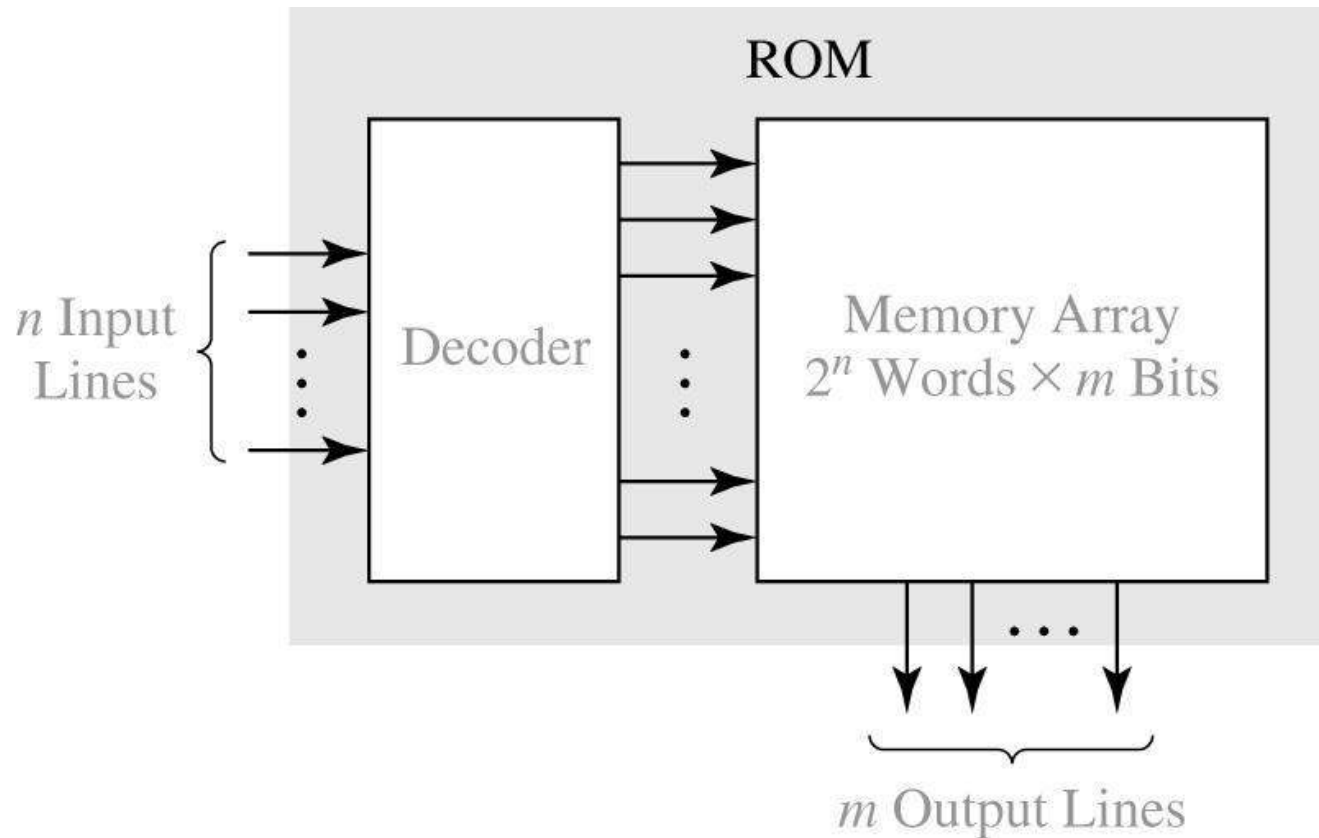

# An 8-Word x 4-Bit ROM

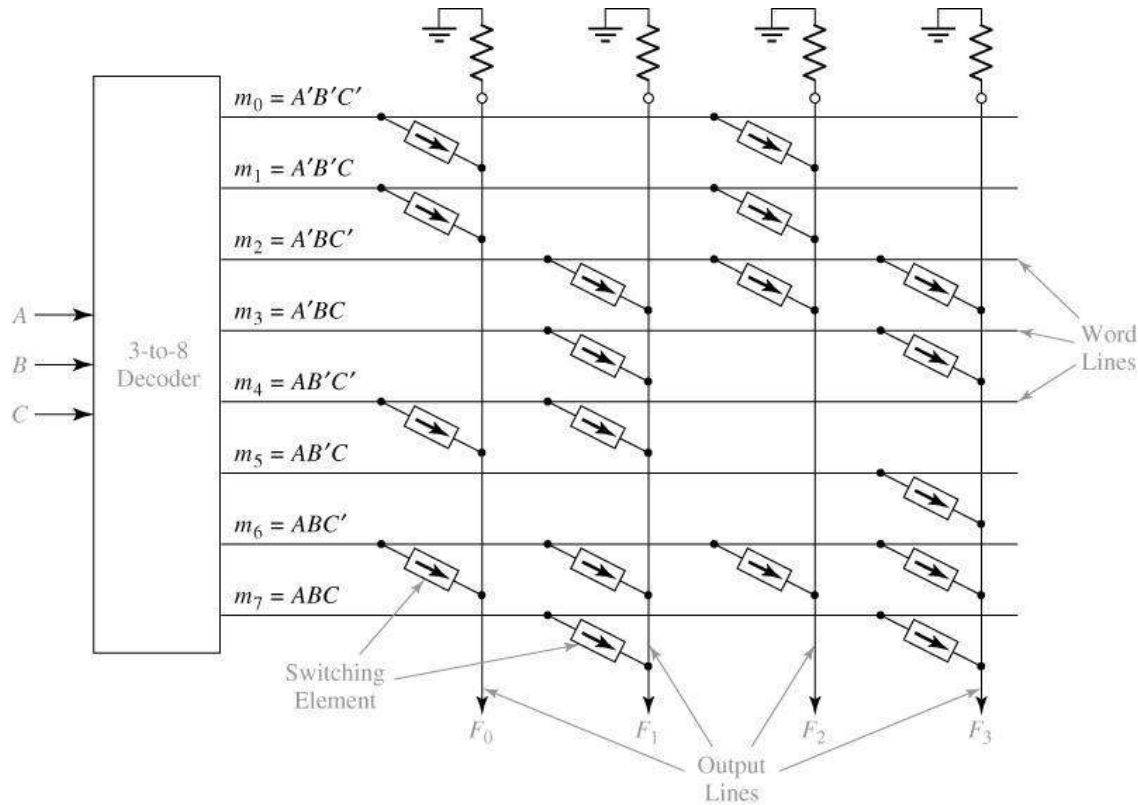

$$F_0 = \sum m(0,1,4,6) = A'B' + AC'$$


$$F_1 = \sum m(2,3,4,6,7) = B + AC'$$

$$F_2 = \sum m(0,1,2,6) = A'B' + BC'$$


$$F_3 = \sum m(2,3,5,6,7) = AC + B$$
 
# ROM

- **programmable versions of the conceptional AND and OR gate**
  - connections are made
    - **during manufacturing**, when physically connect two lines whenever a connection is desired
    - **in the field**, when burn the fuse between an input line and a gate line whenever a connection is not desired




# 16 × 4 ROM

 

# Designing with Read-Only Memories

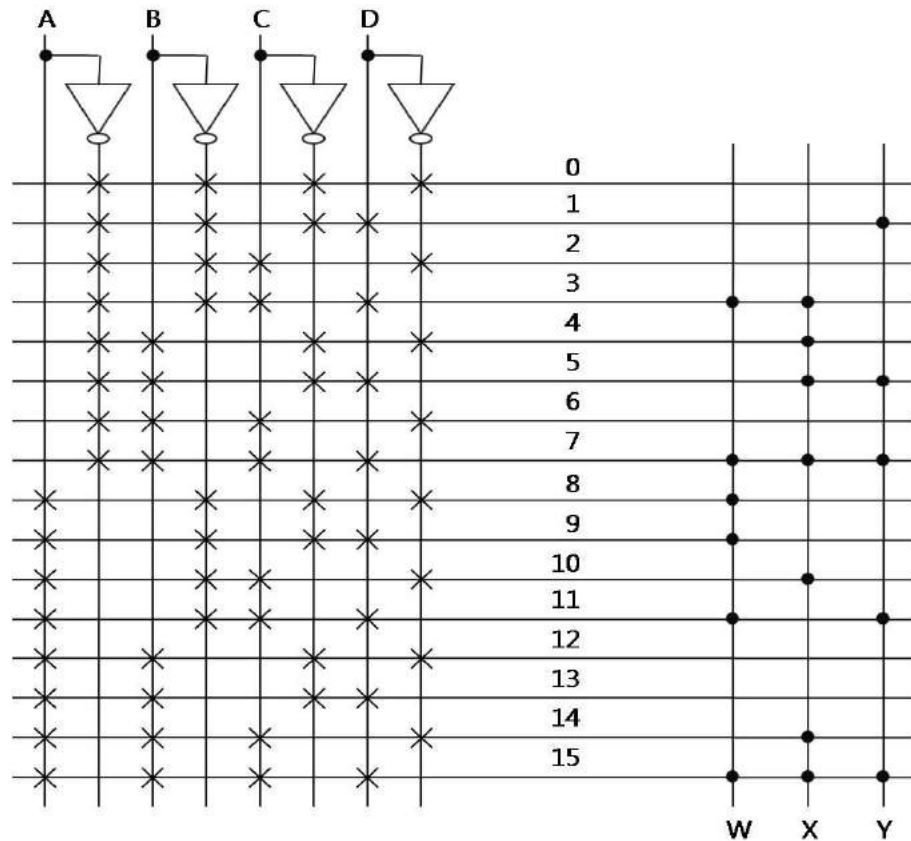
- Example 4.7

$W(A, B, C, D) = \Sigma m(3, 7, 8, 9, 11, 15)$ ,  $X(A, B, C, D) = \Sigma m(3, 4, 5, 7, 10, 14, 15)$ ,  $Y(A, B, C, D) = \Sigma m(1, 5, 7, 11, 15)$




# Hexadecimal to ASCII Code Converter

Input				Hex	ASCII Code for Hex Digit						
W	X	Y	Z	Digit	A <sub>6</sub>	A <sub>5</sub>	A <sub>4</sub>	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>
0	0	0	0	0	0	1	1	0	0	0	0
0	0	0	1	1	0	1	1	0	0	0	1
0	0	1	0	2	0	1	1	0	0	1	0
0	0	1	1	3	0	1	1	0	0	1	1
0	1	0	0	4	0	1	1	0	1	0	0
0	1	0	1	5	0	1	1	0	1	0	1
0	1	1	0	6	0	1	1	0	1	1	0
0	1	1	1	7	0	1	1	0	1	1	1
1	0	0	0	8	0	1	1	1	0	0	0
1	0	0	1	9	0	1	1	1	0	0	1
1	0	1	0	A	1	0	0	0	0	0	1
1	0	1	1	B	1	0	0	0	0	1	0
1	1	0	0	C	1	0	0	0	0	1	1
1	1	0	1	D	1	0	0	0	1	0	0
1	1	1	0	E	1	0	0	0	1	0	1
1	1	1	1	F	1	0	0	0	1	1	0

 

# ROM realization of code converter

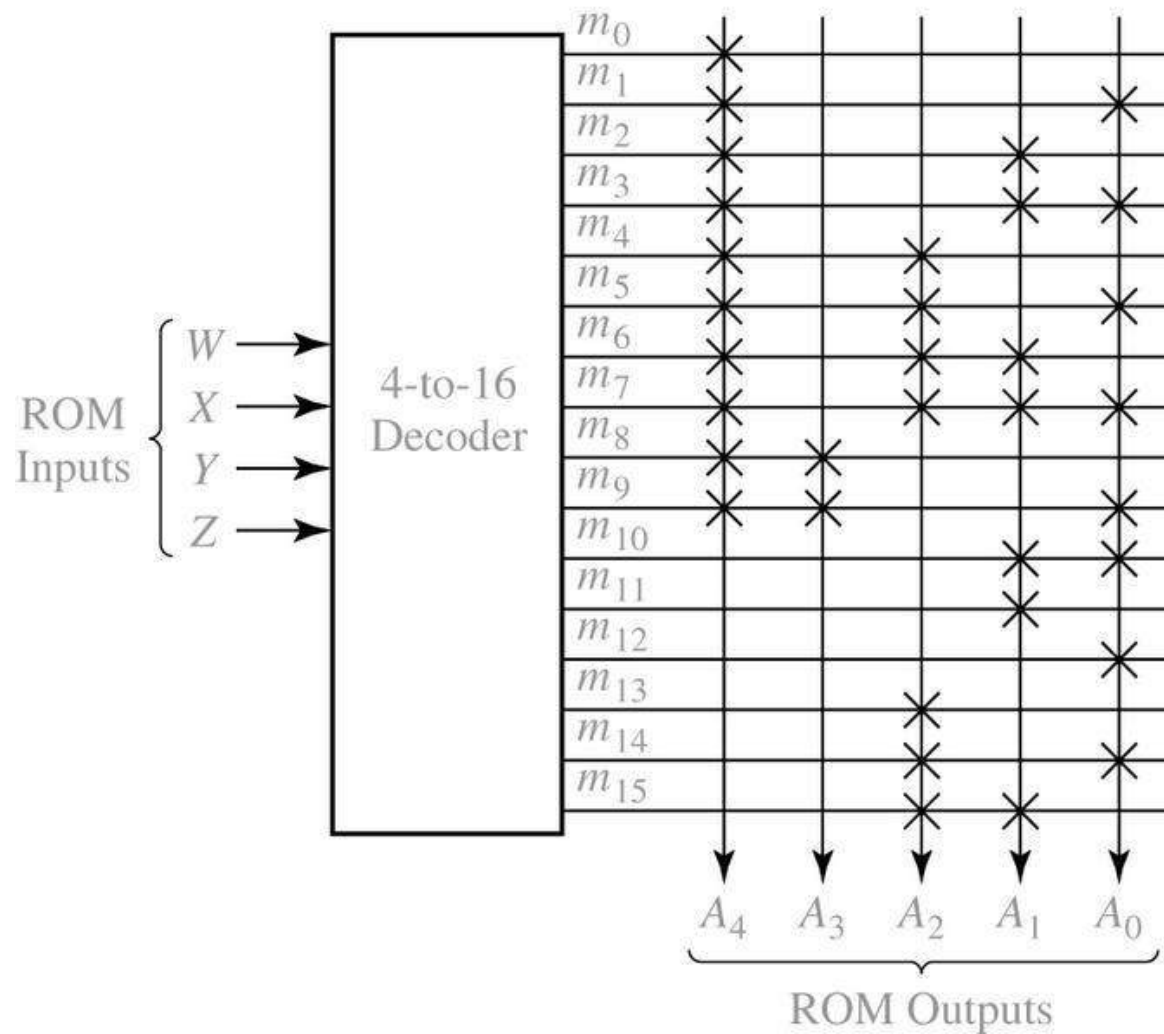



# PROGRAMMABLE LOGIC ARRAYS

---

## ▪ ROMs

- have only a small number of 1's, so many of the words have a value of 0  
⇒ **programmable logic arrays (PLAs) minimize this waste**

## ▪ PLAs differ from ROMs in the address decoder


- instead of a full decoder, use a programmable decoder (AND array), which can be programmed to decode only those words that have a nonzero content
- programmable output array used whenever to complement the output values

## ▪ Advantage of PLAs

- **no less flexible than ROMs**
- more efficient in their implementation of **random logic**
- used more often for the implementation of **control logics**, whereas ROMs are used most frequently for tables of coefficients, startup programs, test vectors, and other random data

# Programmable Logic Devices

- Programmable Logic Array Structure

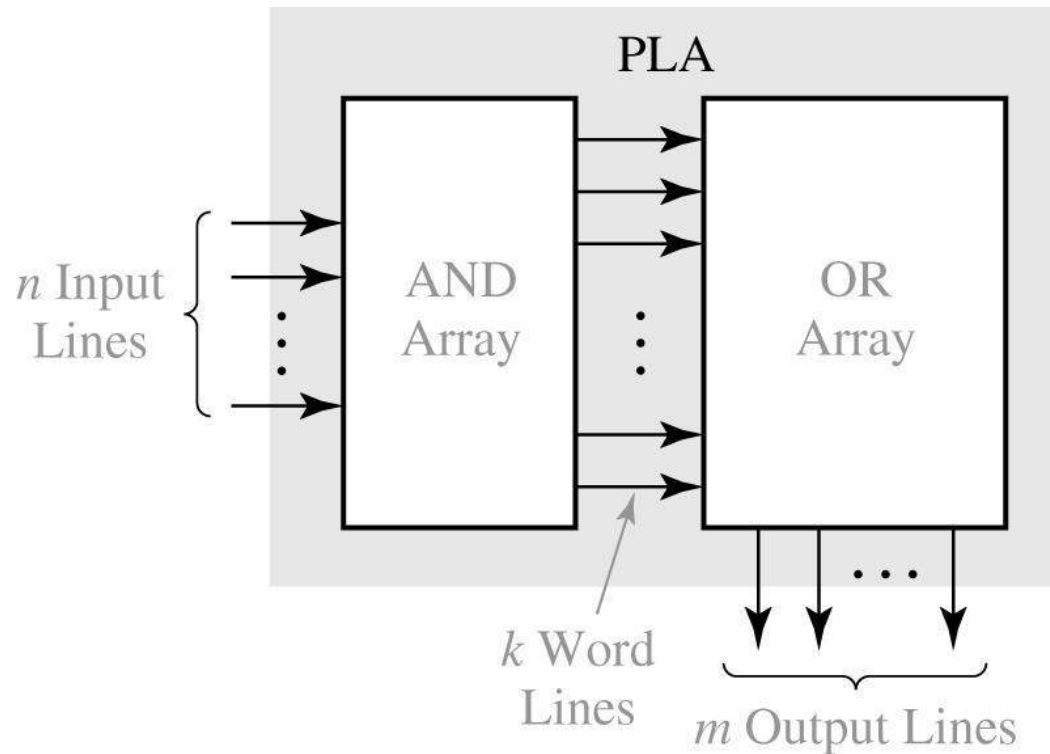

# PLA implementation of the full adder

$A_3$	$A_2$	$A_1$	$A_0$	$F_3$	$F_2$	$F_1$	$F_0$
	$x_i$	$y_i$	$c_i$			$s_i$	$c_{i+1}$
X	0	0	0	X	X	0	0
X	0	0	1	X	X	0	1
X	0	1	0	X	X	0	1
X	0	1	1	X	X	1	0
X	1	0	0	X	X	0	1
X	1	0	1	X	X	1	0
X	1	1	0	X	X	1	0
X	1	1	1	X	X	1	1


$x_i y_i$	00	01	11	10
$c_i$				
0		1		1
1	1		1	

$$S_i = x_i' y_i' c_i + x_i' y_i c_i' + x_i y_i' c_i' + x_i y_i c_i$$

$x_i y_i$	00	01	11	10
$c_i$				
0			1	
1		1	1	1

$$c_{i+1} = x_i y_i + x_i c_i + y_i c_i$$

# PLA implementation of full-adder

 

# Designing with Programmable Logic Arrays

## • Example 4.8

•  $W(A, B, C, D) = \sum m(3, 7, 8, 9, 11, 15)$ ,  $X(A, B, C, D) = \sum m(3, 4, 5, 7, 10, 14, 15)$ ,  $Y(A, B, C, D) = \sum m(1, 5, 7, 11, 15)$

A B		00	01	11	10
C D	00				1
	01				1
	11	1	1	1	1
	10				

W

A B		00	01	11	10
C D	00		1		
	01		1		
	11	1	1	1	
	10			1	1

X

A B		00	01	11	10
C D	00				
	01		1	1	
	11		1	1	1
	10				

Y

- $W = AB'C' + CD$
- $X = A'BC' + A'CD + ACD' + \{BCD \text{ or } ABC\}$
- $Y = A'C'D + ACD + \{A'BD \text{ or } BCD\}$

# PLA example

C D \ A B		00	01	11	10
		00	01	11	10
C D	00				1
	01				1
	11	1	1	1	1
	10				

W

C D \ A B		00	01	11	10
		00	01	11	10
00			1		
01			1		
11	1	1	1		
10				1	1

X


C D \ A B		00	01	11	10
		00	01	11	10
00					
01	1	1			
11		1	1	1	
10					

Y


- $W = AB'C' + A'CD + ACD$
- $X = A'BC' + ACD' + A'CD + BCD$
- $Y = A'C'D + ACD + BCD$

- This solution only uses seven terms instead of eight or nine.


# solution

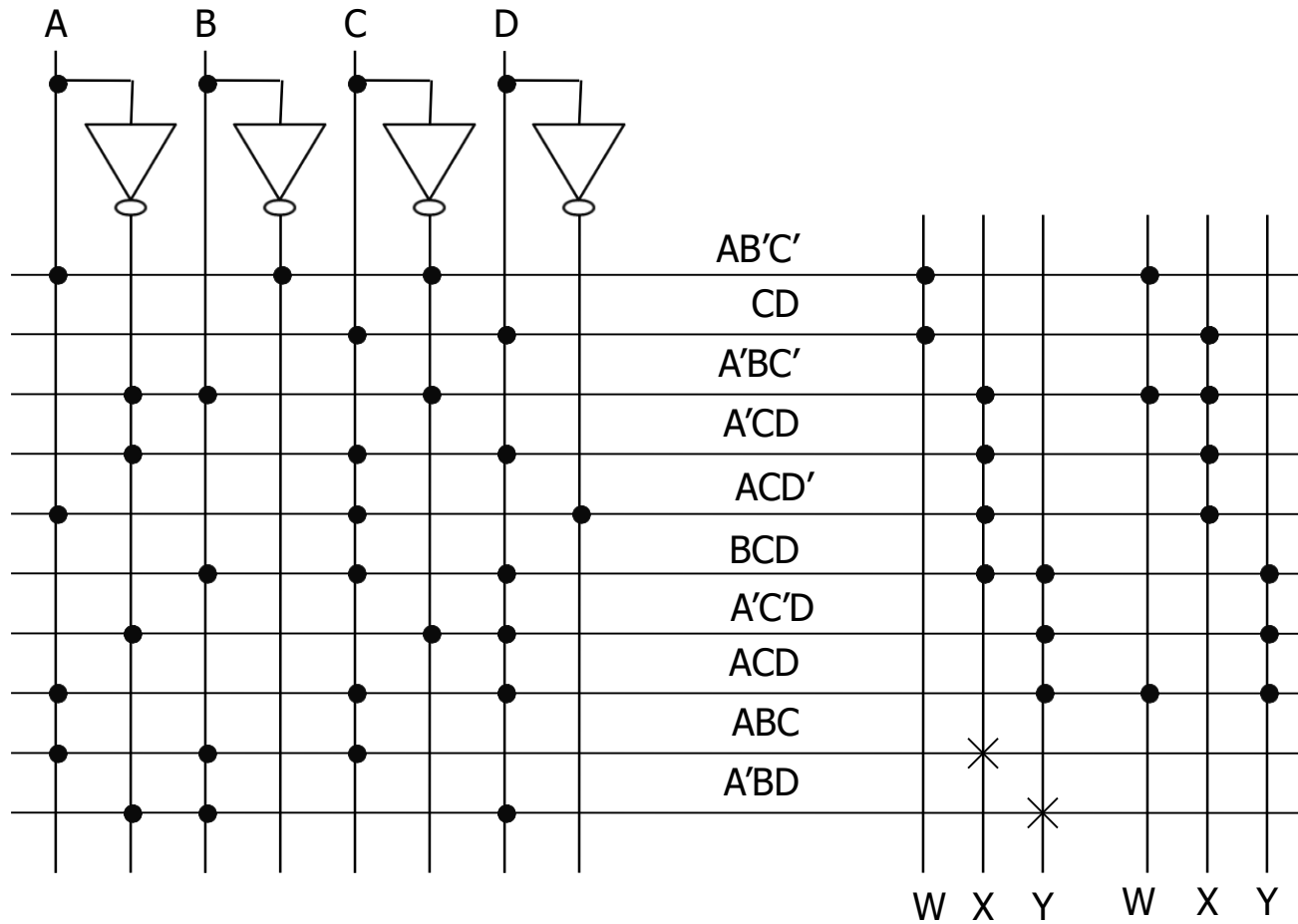

# Programmable logic array (PAL) devices

 


(a) Unprogrammed



 


(b) Programmed



 

## Example 4.11

   

- The three green terms are essential prime implicants of each function but other two are not.

- $f = a'b'c' + a'c'd + b'c'd + abd' + bcd'$
- $g = a'b'c' + a'c'd + b'c'd + abc + acd'$
- $h = a'b'c' + a'c'd + b'c'd + a'cd' + b'cd'$

# PAL solution

